

13. Computer Arithmetic


– Adders and Subtractors

Manchester Carry Chain

- Reuses P, G logic for intermediate carry signals
 - Not suitable for CMOS gates
 - Transistor level (pre-charge internal nodes)
 - Good for up to 16 bits

Carry-bypass adder

 - Idea is to bypass carry logic using P signals
- The local carry chain could be “ripple carry adder”



- Structure
 - Could be static, dynamic, pass transistor
 - Bypass logic determines: “pass” or “kill/generate”?


Carry-bypass adder: structure

Timing (Critical path shown in different color):

1-Setup

2-Local carry generate/kill, MUX select line ready


 
3- C_0 - C_{16} carry propagate (if applicable)



Carry-bypass adder: timing of sub-block


For an intermediate stage, after setup:

- If in *pass* mode
 - Local carry vector computes intermediate carries (possibly incorrectly)
 - At the same time, mux selection set to pass
 - When input carry arrives, intermediate carries might be recomputed
 - Meanwhile, input carry is sent to Cout
- If *not pass* mode (assume bit 10 generates)
 - Local carry vector computes intermediate carries (bits 10, 11 correct)
 - At the same time, mux selection set to local
 - Meanwhile, output carry is sent to Cout correctly
 - When input carry arrives, intermediate carries C_8 and C_9 (S_8, S_9, S_{10}) will be recomputed correctly

  

Carry-bypass adder: timing
 
$$\text{Delay} = t_{\text{setup}} + \max \{ t_{\text{select}}, 4 \times t_{\text{FA}} \} + 3 \times t_{\text{mux_pass}} + 4 \times t_{\text{FA}}$$




Carry-bypass adder: pros and cons

Speed:


- Faster than ripple adder
- Still linear!

Area overhead:

 - Mux (setup?)
- Not worth for small adders ($N < 8$)
- 10-20% for large adders




Carry-select adder: idea

 


Similar to bypass

- Instead of “waiting” for the input carry, “precompute” the carry output
- Compute C_{i+k} for both cases $C_i=0$ and $C_i=1$
- When C_i arrives, select the appropriate result
- Sum computed in one step after the intermediate carry signals are ready

Linear carry-select adder: structure

 

Linear carry-select adder: timing

 

$$\text{Delay} = 3 + 1 + 1 + 1 + 1 = 7 \text{ (16 bits)}$$

Square root carry select adder: idea

Later stages have to wait for the multiplexers in the earlier stages


Why not give them bigger chunks of data to compute?

- Balances the delay paths
- Sub-linear delay

Square root carry select adder: structure

Assuming the following delays:

- Setup=1, carry propagate=1/bit, mux=1

 

Delay from all paths = 8 (20 bits)


Carry select adder: trade-offs

Area overhead:

- An additional carry path and a multiplexer (not the whole adder)
- About 30% more than a ripple-carry

Delay

- Sub-linear (we can beat that too!)

 

Crude adder speedup




Ripple	(Slowest)
Carry-Lookahead	
Carry-Select	
Manchester	
Transmission Gate	(Faster)
Block Carry-Lookahead	

Use block carry lookahead for floating-point ALU's


Subtractor

- Subtractors are the same as adders in construction
- Subtraction is normally done using 2's complement numbers
 - The subtrahend has to be converted to 2's complement form
 - Add the 2's complemented subtrahend to the minuend

Subtractor circuit

 

Adder/Subtractor circuit

 

If $C_{in} = 0$, the circuit will act as adder, If $C_{in} = 1$, the circuit will act as subtractor

Carry logic

<i>A</i>	<i>B</i>	<i>Cin</i>	<i>Sum</i>	<i>Cont</i>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

When coding addition as $A+B$,
we don't know C_{in} at MSB, but we know
 $Sum[7]$

Carry is set at MSB if:

$$A[7] \& B[7] \mid B[7] \& \sim Sum[7] \mid \\ A[7] \& \sim Sum[7]$$

In subtraction $A-B$, complement $B[7]$

Detection of 2's complement overflow

<i>A</i>	<i>B</i>	<i>Cin</i>	<i>Sum</i>	<i>Cout</i>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Overflow occurs in addition if the signs of both operands are the same, but the result sign is different, i.e.

**$A[7] \& B[7] \& \sim \text{Sum}[7] \mid$
 $\sim A[7] \& \sim B[7] \& \text{Sum}[7]$**

In subtraction B-A, invert A[7]

Some processors (MIPS, Arm) set Carry and Overflow flags

```

RADD : begin
    V = a[7] & b[7] & ~sum[7] | ~a[7] & ~b[7] & sum[7];
    C = a[7] & b[7] | a[7] & ~sum[7] | b[7] & ~sum[7];
end
RSUB : begin
    V = a[7] & ~b[7] & ~sum[7] | ~a[7] & b[7] & sum[7];
    C = a[7] & ~b[7] | a[7] & sum[7] | ~b[7] & sum[7];
end
    
```