


15: Computer Arithmetic

- Shifting and complex arithmetic

Shift and Rotate operation


- Used in microprocessor and encryption algorithm
 - Shift left by one place = multiply by 2
- If fixed shift: simply wire the inputs to the correct output position
- Variable shift
 - One bit shifter
 - Barrel shifter
 - Logarithmic shifter

One bit shifter

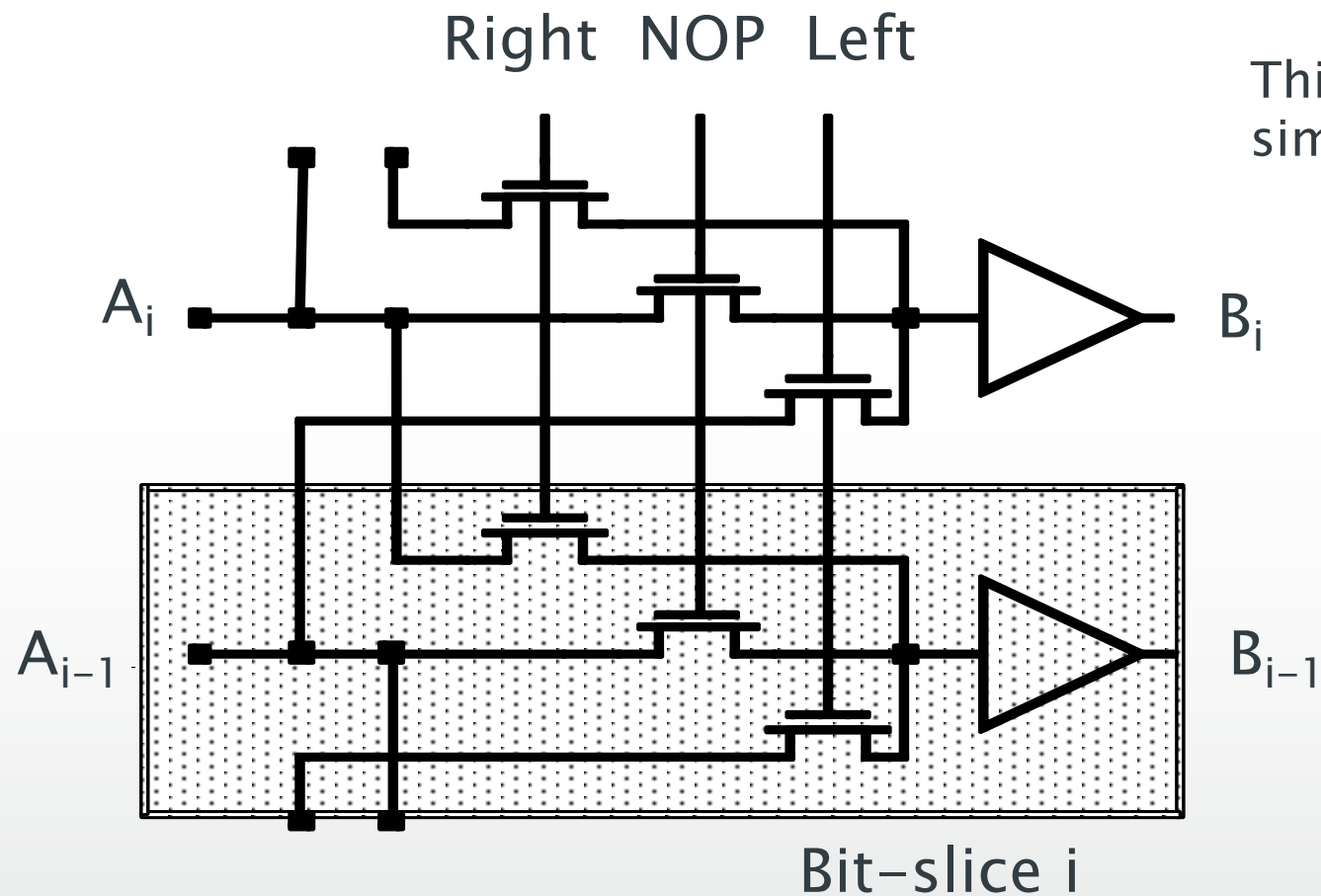


Simple N-bit shifter

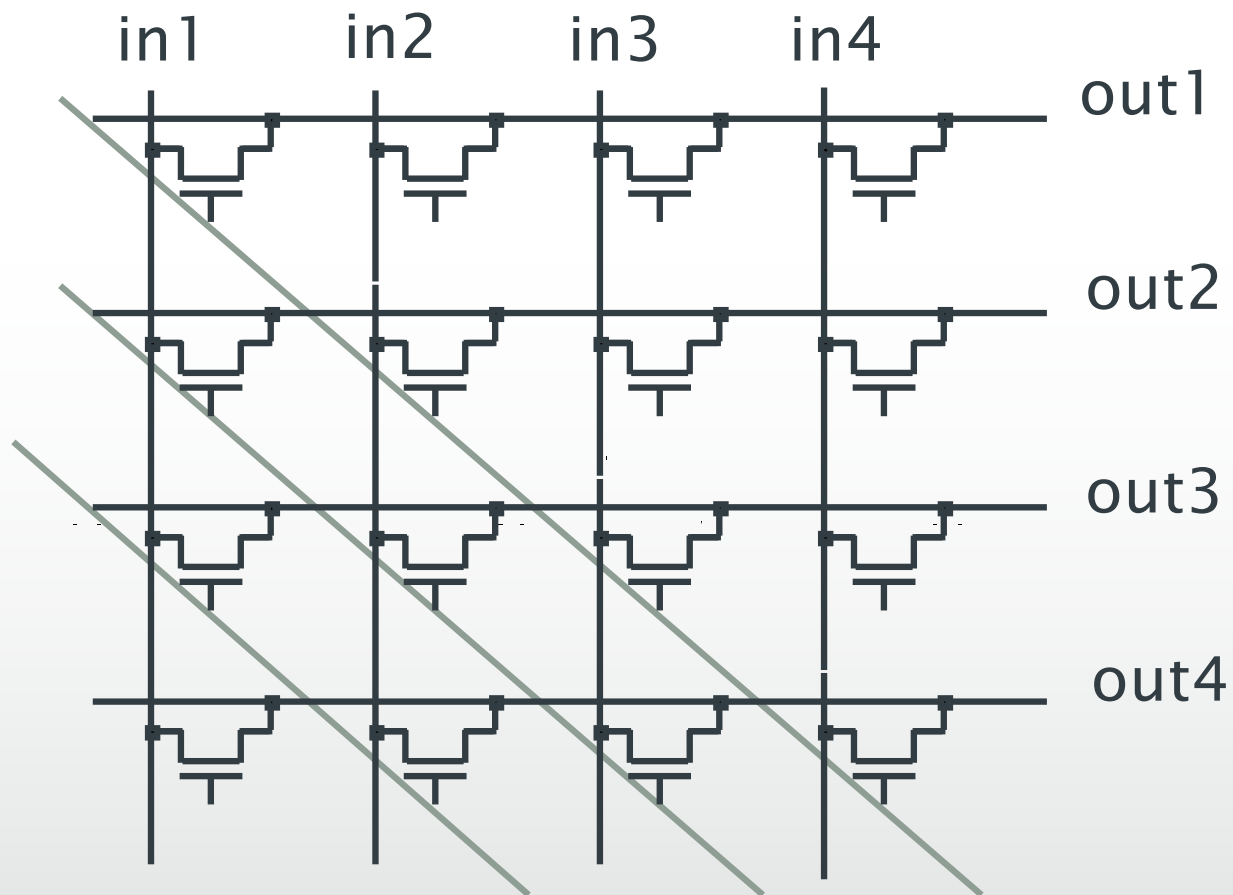- Quadratic number of transistors: one transistor switch per path




Barrel shifter

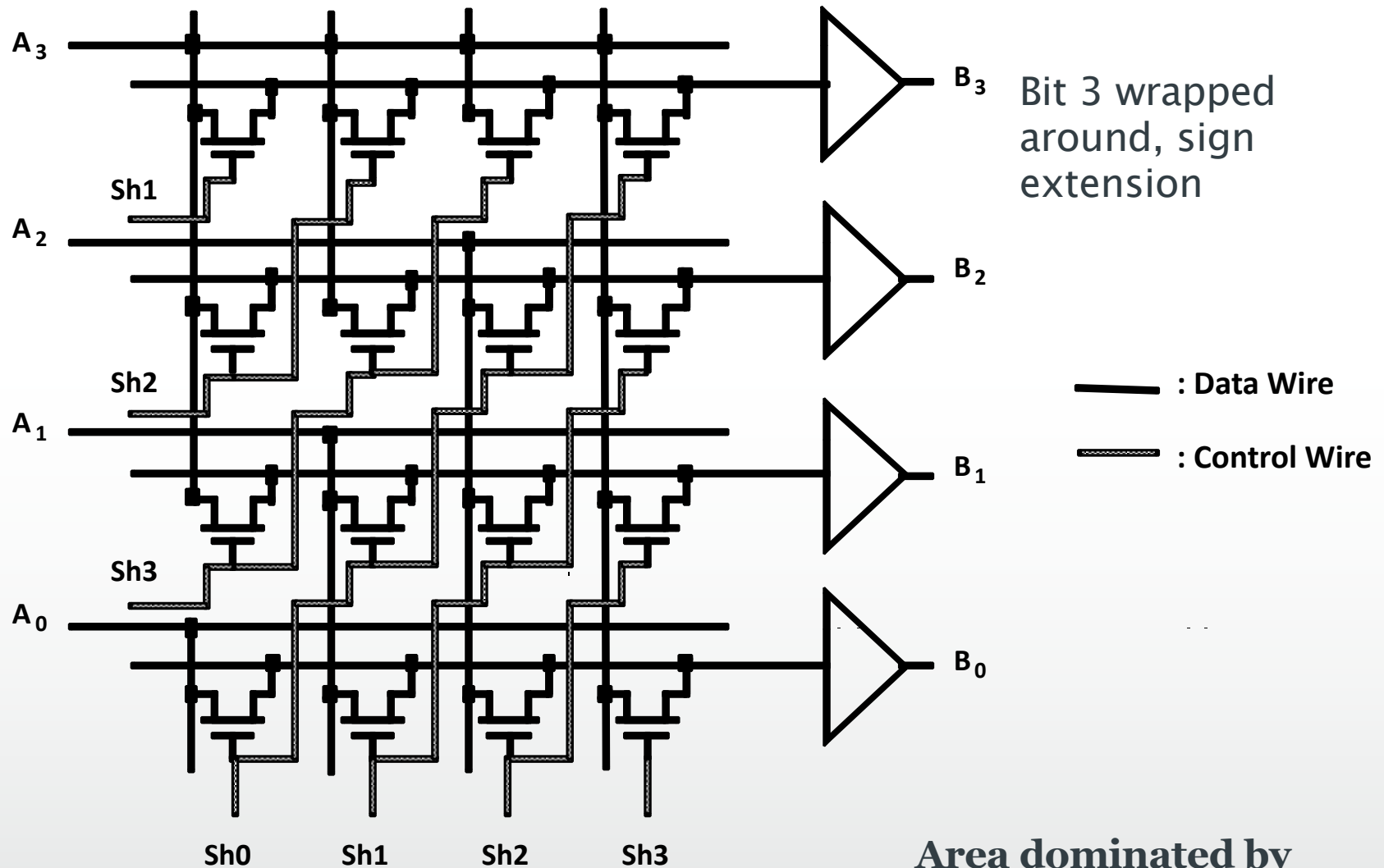

Area dominated by
wiring


Logarithmic shifter

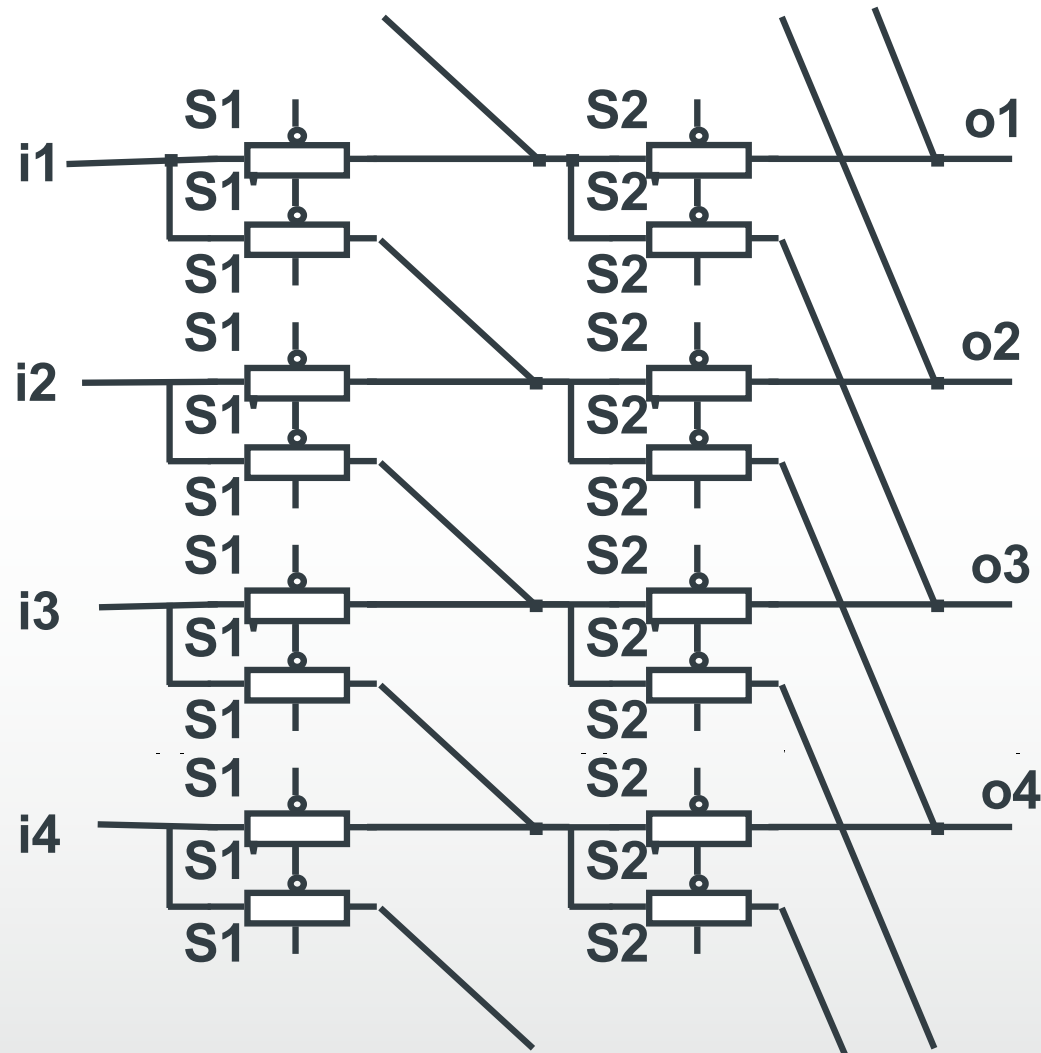

Shift by 1 place,
then by 2 places


Simplified structure
but more stages
(greater delay)

Programmable shifter example: 16-bit

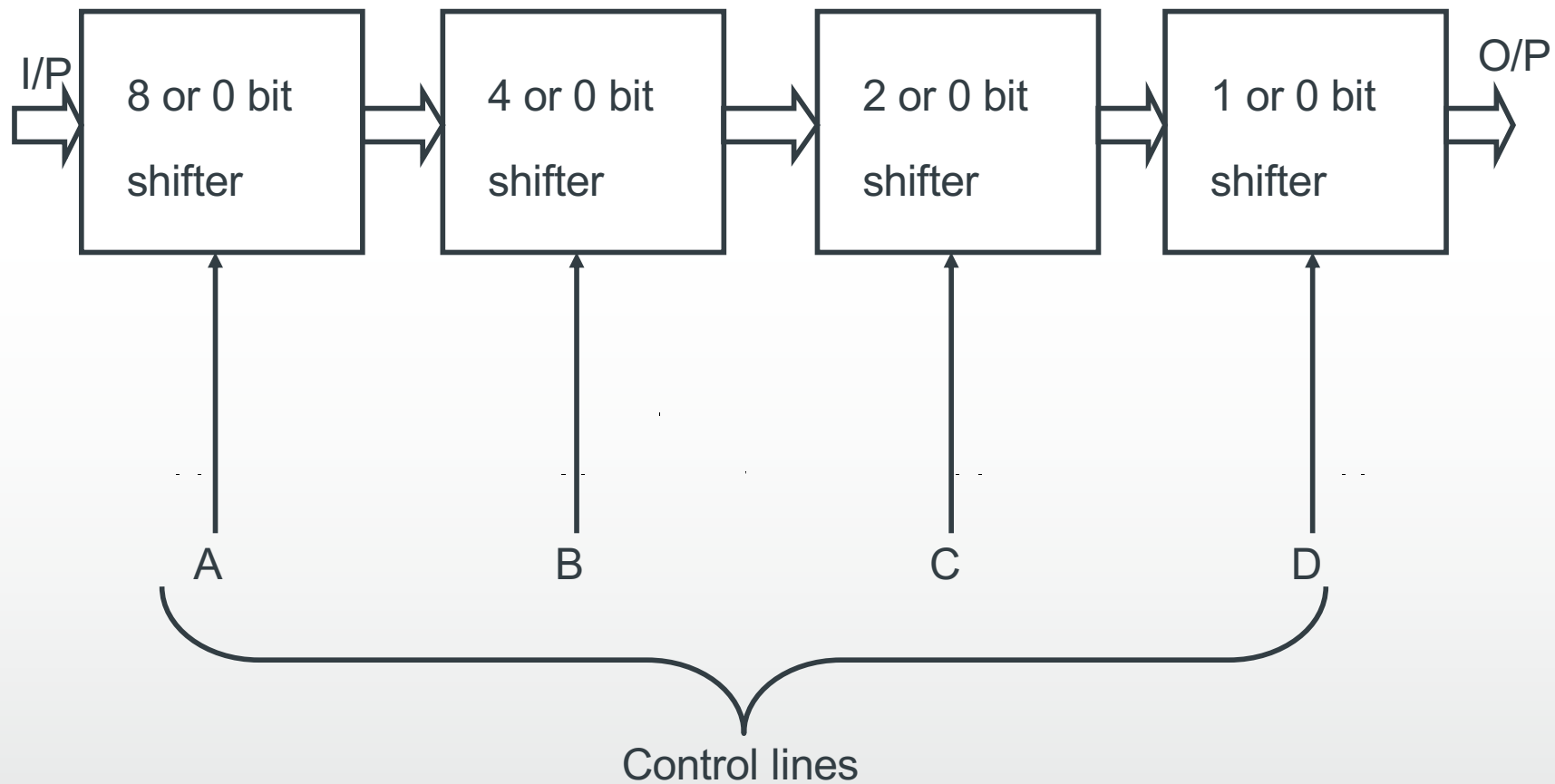

Multiplication using shifter
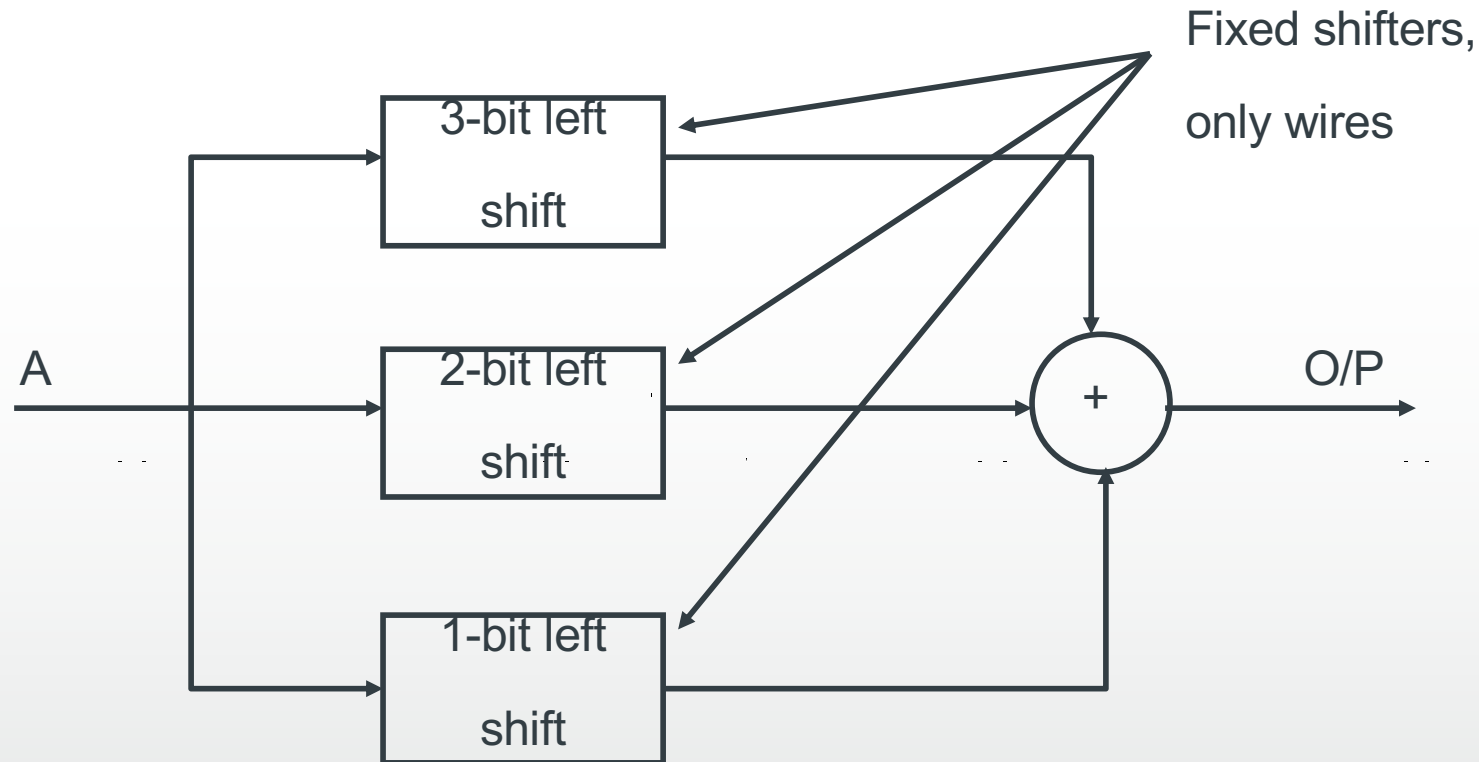
$$A \times 14 = A (1110) = A (2^3 + 2^2 + 2^1)$$



Shifter: summary

- Trade-offs between area and delay
 - Barrel shifter: fastest $O(1)$, N^2 transistors
 - Logarithmic shifter: $O(\log N)$, $N \log N$ transistors
 - One bit shifter: $O(N)$, N transistors
- Barrel shifter: wire dominated circuit
- Note. Floating point arithmetic uses shifters a lot to align mantissas

ALUs: Summary

- ALU has to implement
 - Addition (2's complement covers subtraction)
 - Shifting
 - Bitwise logical operations
 - Comparisons can be done by subtraction
- Extended ALU may include
 - Multiplication/Division
- RISC-V allows us to include custom instructions
 - e.g. complex arithmetic

Complex numbers and addition

- Complex numbers have real part and imaginary part


$x = a + jb$, a = real part, b = imaginary part

BUT both are just NUMBERS – complex number represents a vector with amplitude $\sqrt{a^2+b^2}$ making a phase angle $\theta = \tan^{-1}(b/a)$ with the real axis

So use two separate bus for them – b-bit complex number = b-bit real number and b-bit imaginary number $\equiv$ 2-b bit wordlength

But keep the convention, i. e., add real part with real part and imaginary part with imaginary part – don't mix them
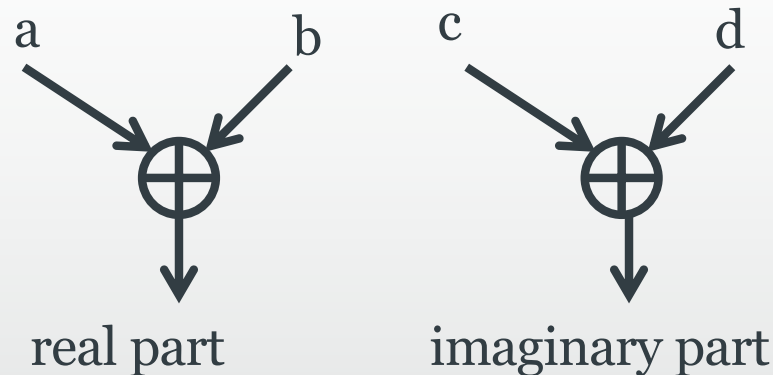
$$(a + jb) + (c + jd) = (a + c) + j(c + d)$$



The complexity of a b-bit complex adder is 2b full adders


Multiplication of complex numbers

- Addition is straightforward, what about multiplication?

$$x = a + jb, y = c + jd$$

$$xy = (ac - bd) + j(ad + bc) = A + jB$$

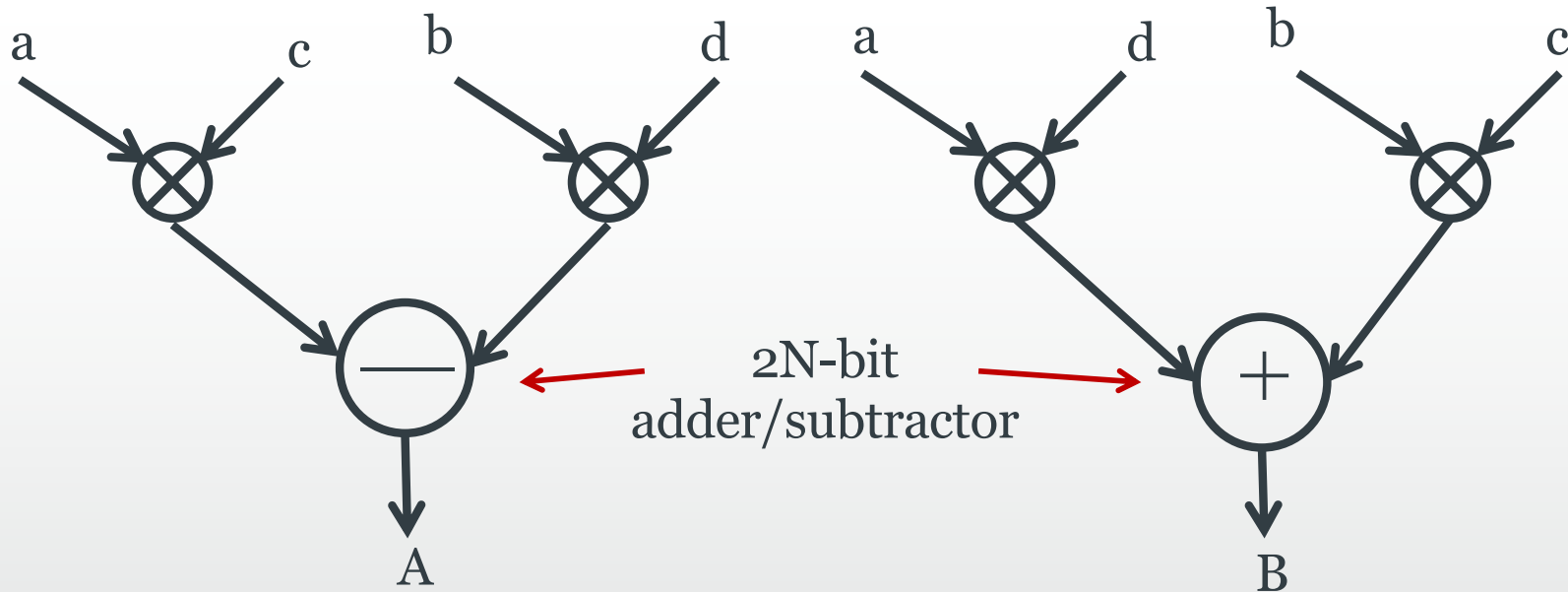- So one complex multiplication in reality is 4 real multiplications + two addition/subtraction



Multiplication of complex numbers

- Overall complexity?

1 N-bit real multiplier = $N(N-2)$ full adders, N half adders and N^2 AND gates

Total complexity = $4 [N(N-2) \text{ full adders} + (N/2) \text{ full adders} + N^2 \text{ AND}] + 2$
($2N$ -bit) full adders = $2N(2N - 1)$ full adders + N^2 AND gates

-

- Can we reduce it?

$$xy = (ac - bd) + j(ad + bc) = [c(a + b) - b(d + c)] + j [d(a - b) + b(c + d)]$$

We can reuse the term $b(c + d)$ resulting in overall complexity of 3 N-bit adders, 3 $(N+1)$ -bit multipliers and 2 $(2(N + 1))$ -bit adders $\approx (1/2)[6N^2 + 17N + 5]$ full adders + $3(N+1)^2$ AND gates

Reduced complex multiplier diagram

