

22. Testbenches

22.1 Basic Testbench

What is a testbench?

- Top level module in design, with no ports
- Used for testing and verification
 - the testbench is not synthesised, used in simulation only
- May contain one or more initial blocks with clocks and input waveforms

Typical testbench

```
// Tested module, register with parallel load
// and 3-state output:
module regs (input logic clk, ctrl, load, reset, input logic
[7:0] D, output logic [7:0] Q);

logic [7:0] buf; // buffer memory

always_ff @ (posedge clk)
    if (reset)
        buf <= 8'h00;
    else if (load)
        buf <= D;

// 3-state output
assign Q = (ctrl ? buf: 8'bZZZZ_ZZZZ);

endmodule
```

```
module testbench;

logic[7:0] Q,D;
logic clk,ctrl,load,reset;

// register instance
regs r (.*); //use default size – 8 bits

initial // clock block
begin
    clk = 1'b0;
    forever #10 clk = ~clk;
end;

initial
begin
    D = 8'hAA; // sample data
    ctrl = 1'b1; // drive output
    load = 1'b1; // load D
    reset = 1'b1; // clear register
    #50 reset = 1'b0; // remove reset
    #50 ctrl = 1'b0; // remove ctrl, outputs go hi-z
end; // 2nd initial block

endmodule;
```

Example 2

This module contains two instances of module `regs` with two sets of inputs and outputs and two separate control signals `ctrl1` and `ctrl2`.

Note that the outputs of both registers are wired together to port `Q`

Also note the use of named port mapping


Write a suitable testbench.

As a conflict will occur if both wired outputs are driven at the same time, the testbench should display a message if at least one of the registers does not have its outputs at the high impedance state at any point of time.

```
module tworegs #(parameter n=8) (output logic[n-1:0] Q,  
input logic[n-1:0] D1,D2, input logic clk, ctrl1, ctrl2, load, reset );  
  
// register instances – nb: outputs might  
regs r1 (.Q(Q),.D(D1),.ctrl(ctrl1),.load(load),.reset(reset),.clk(clk));  
regs r2 (.Q(Q),.D(D2),.ctrl(ctrl2),.load(load),.reset(reset),.clk(clk));  
  
endmodule
```

Checking Responses

- Compare with reference

 

- Reference could be behavioural (simulation) model

Testbench 2

```
module testbench;

logic[7:0] Q,D1,D2;
logic clk,ctrl1,ctrl2,load,reset;

// instance of the tworegs module
tworegs r (.*) //use default size – 8 bits

initial // clock block
begin
    clk = 1'b0;
    forever #10 clk = ~clk;
end;

// concurrent assertion to detect if both
// outputs are driven at same time
assert property (@(posedge clk)
    ~ctrl1 | ~ctrl2 )
    else
    $error("bus conflict at time %0t", $time);

...
```

```
...

initial
begin

    D1 = 8'hAA; // data
    D2 = 8'11;
    ctrl1 = 1'b1; // drive output1
    ctrl2 = 1'b0; // disconnect output 2
    load = 1'b1; // load D1,D2
    reset = 1'b1; // clear registers

    #50 reset = 1'b0; // remove reset
    #50 ctrl1 = 1'b0; // remove ctrl1, outputs go hi-z

    //assertion above should now fail:
    #50 ctrl1 = 1'b1; ctrl2 = 1'b1; // both registers driven

end;
```

Synchronising Signals

- Suppose we want to change a signal 10 ns after a rising clock edge:

```
initial // or always?
```

```
begin
```

```
@(posedge clock);
```

```
// wait for clock to change to 1
```

```
#10ns a = a + 1;
```

```
end
```

- It *might* be better to use a nonblocking assignment!

Randomly-Timed Inputs

- "Real World" inputs are random w.r.t. clock
- Need random number generator
- Negative exponential function is a good approximation to random arrival times:

```
#($dist_exponential(seed, 10000));
```


- Need to specify time units

```
timeunit 1ns; timeprecision 100ps;
```

 22.2 Testbench Example

Modular testbench example

- Simple example to illustrate a layered testbench



- Verify a sequential Booth multiplier (DUV)

Top Level

```
module testbooth;

parameter N = 16;

logic signed [N-1:0] ain, bin;
logic signed [2*N-1:0] qout;
logic clk, load, n_reset;
logic ready;

clock_gen #(10.0, 10.0) c0 (.*) ;
stimulus s0 (.*) ;
booth #(N, N, 2*N) b0 (.*) ; //DUV
verify v0 (.*) ;

endmodule
```

Booth Multiplier

```
module booth #(parameter AL = 8, BL = 8, QL = AL+BL)
  (output logic [QL-1:0] qout, output logic ready,
   input logic [AL-1:0] ain, input logic [BL-1:0] bin,
   input logic clk, load, n_reset);
```

```
  .
  .
  .
```

```
endmodule
```

Clock generator

```
module clock_gen
  #(parameter ClockFreq_MHz = 100.0,   ResetWidth=10.0)
    (output logic clk, n_reset);
  timeunit 1ns;
  timeprecision 100ps;

  parameter ClockHigh = (500.0)/ClockFreq_MHz;

  initial
    begin
      n_reset = '1;
      clk = '0;
      #ResetWidth n_reset = '0;
      #ResetWidth n_reset = '1;
      forever #ClockHigh clk = ~clk;
    end

endmodule
```

Note that this is a module

Stimulus

```
module stimulus #(parameter NA = 16, NB = 16)
    (output logic signed [NA-1:0] ain,
     output logic signed [NB-1:0] bin,
     output logic load);

initial begin
    #30ns ain = -10; bin = 10;
    #10ns load = '1;
    #10ns load = '0;
end

endmodule
```

Verify

```
module verify #(parameter AL = 8, BL = 8, QL = AL+BL)
  (input logic signed [QL-1:0] qout,
   input logic ready,   input logic signed [AL-1:0] ain,
   input logic signed [BL-1:0] bin, input logic clk, load);


  always @(posedge clk)
    $display("%d * %d gives %d", ain, bin, qout);

endmodule
```

- Could also check that ready flag is asserted at the right time (after AL cycles)
- SystemVerilog also has assertions
 - We can assert that a property will be true in a particular cycle
 - Syntax is different to synthesisable code, but time dependencies can be concisely expressed

22.2 Testbench Strategies

The Basic Testbench

 

Verification Plan

- As the design develops, do you want to keep testing the same things?
 - Check to see that the design has not been broken (regression testing)
 - Check new things
- One simulation run? Or a number of smaller simulations?
- Need to write a verification plan – what to verify, when, how

Divide and Conquer

- Your design isn't one huge monolithic block
- Why should the testbench be like that?
- Issues:
 - Verification plan probably requires many different tests
 - Need to test several versions of the design
 - Create environment around the design
- Objectives:
 - Flexibility
 - Low-effort maintenance and enhancement
 - Reliability
 - Re-use

Monolithic Testbenches are Inflexible

- Consider what would need to be changed to run different test cases
 - *test case* = group of tests required by one aspect of the verification plan, run as one simulation
- Stimulus generator and file output writers would need to change
- Top-level testbench then changes to accommodate them

Package Useful Functionality


- High-level component models for other parts of the system
- Stimulus generator
- Output checker
- Logging and monitoring
- Utility functions (application-specific calculations)

22.3 Verification Methodologies

Standards

- Universal Verification Methodology (UVM) is an industry standard for verifying designs.
 - SystemVerilog class library for simulation
- cocotb is an open source approach backed by Synopsys, Cadence, Siemens, Aldec
 - Python class library
- Similar objectives, but very complex

Testbench structure

 

SystemVerilog constructs

- class – Test, Env, Scoreboard, Driver, Monitor are defined as SystemVerilog classes (encapsulation)
- interface – used to group signals
 - virtual interface – group signals between objects and modules